

In the same circuit, when will the first maximum of the oscillation current occur? We say $t = 0$ when the switch is turned to b .

- a) $t = 0$
- b) $t = \frac{T}{4}$
- c) $t = \frac{T}{2}$
- d) $t = \frac{3T}{4}$
- e) Not enough information to decide
- f) I don't know

